

LZ1AQ Amplifier Project

Making It Up

John VE6EY

<http://play.fallows.ca>

Introduction

Full credit to [Chavdar Levkov LZ1AQ](#) for his [Wideband Active Small Magnetic Loop Antenna Amplifier Design](#).

As part of my exploration of wideband loop antennas, I built Chavdar's 2011 amplifier design. First I tested the circuit on a breadboard. Second, I designed a PCB to implement the amplifier using surface mount components.

The amplifier is mounted in a 1 meter loop, and connected to the shack through CAT7 cable. An optional balun is used at the receiver input.


Here is the project documentation.

73 John VE6EY
Calgary, Alberta
May 2019



References

- [Original LZ1AQ Design](#)
- [Obtain my PCB Design from OSH Park](#)


Schematic

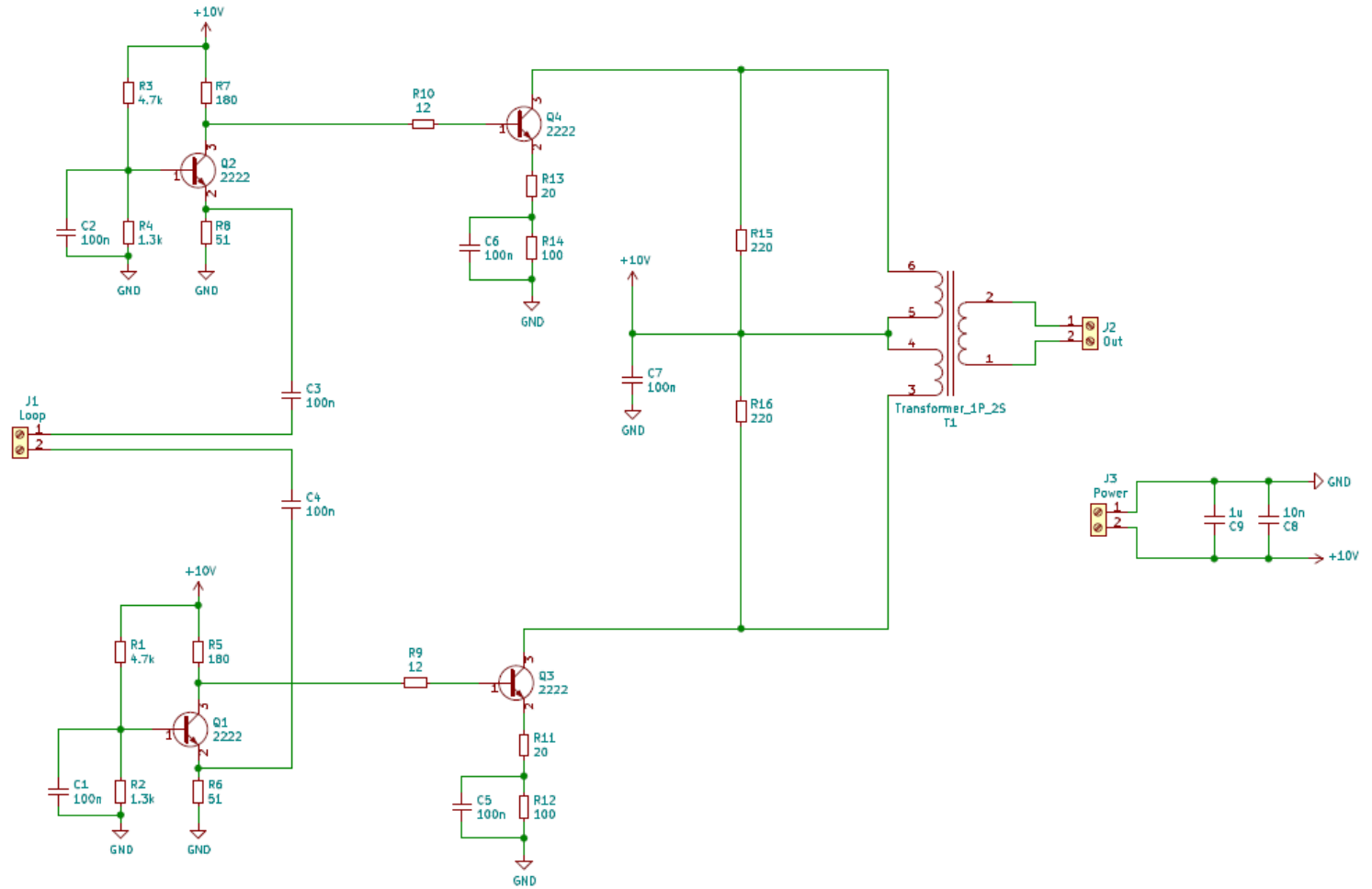

Breadboard

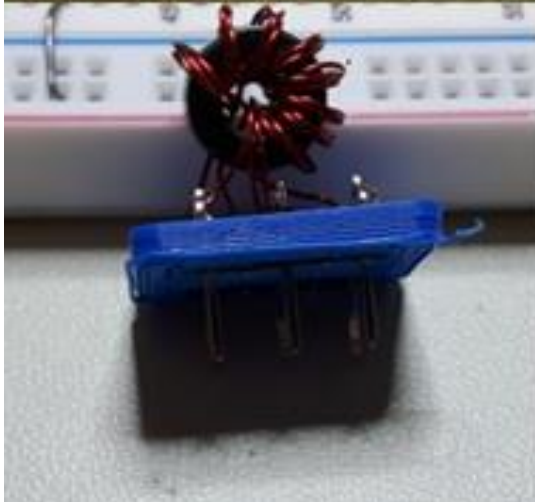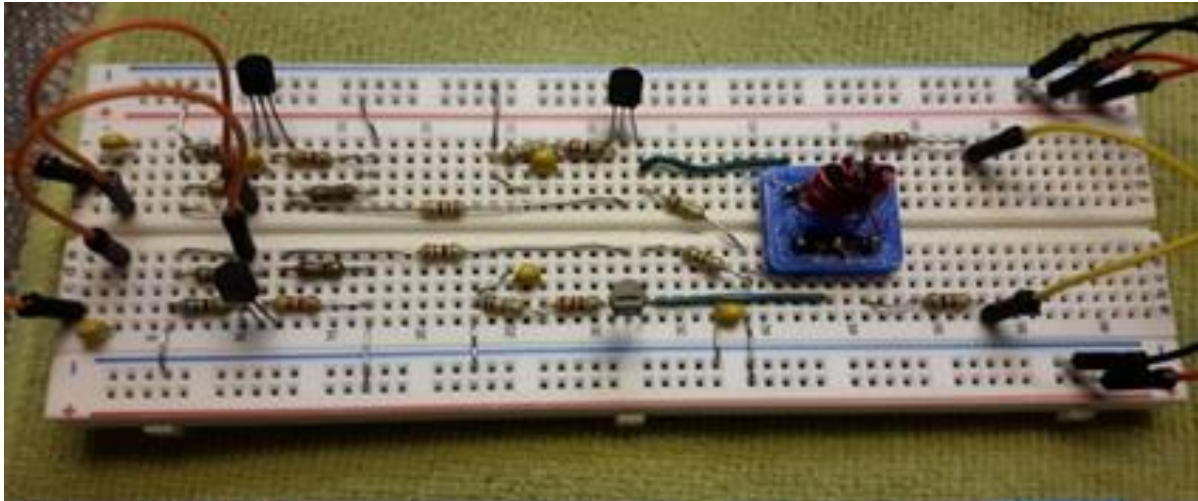


PCB Board

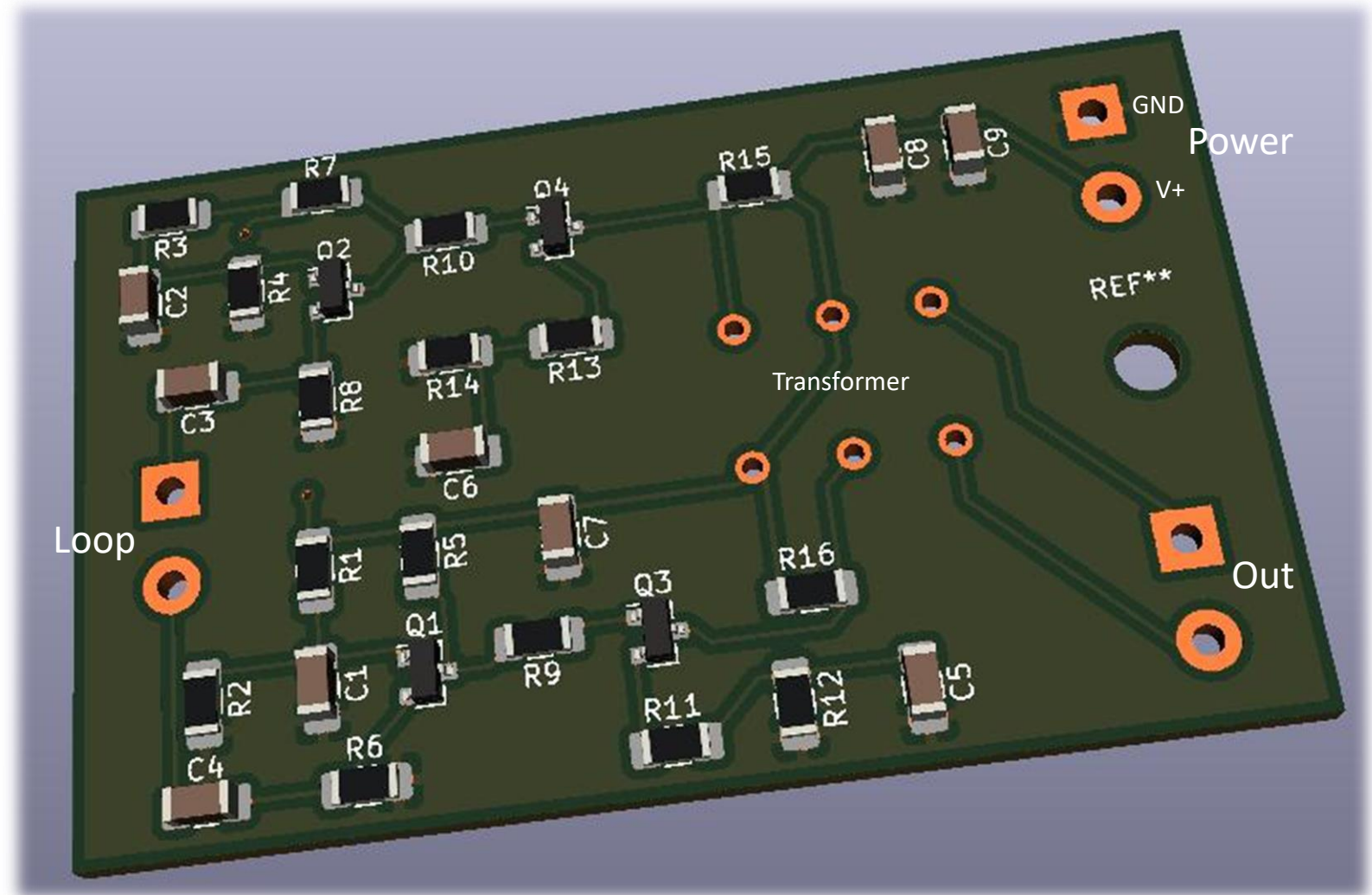

Bill of Materials


Part	Description	Cost
PCB	LZ1AQ_2 PCB from OSH Park, 3 for \$17.50	6.00
Transistors	(4) MMBT2222A-7-F, SOT23 version of 2N222A, 40V 300mW	1.00
Resistors	(2) Each of 12, 20, 51, 100, 180, 220, 1.3K and 4.7K Ω SMD 1206 5% ¼ Watt	0.50
Capacitors	(7) 100nF (1) 1uF (1) 10nF SMD 1206 20% 50V	3.00
Transformer	Eight trifilar turns of magnet wire on a FT37-43 core. Mounted on a modified DIP Socket, row spacing 7.62 mm, pin pitch 2.54 mm. (Use 16 pin DIP and cut off pins not needed.)	0.50
Hardware	(3) Screw Terminals with 5.08 mm pin spacing	0.50

US Dollars, Total \$11.50

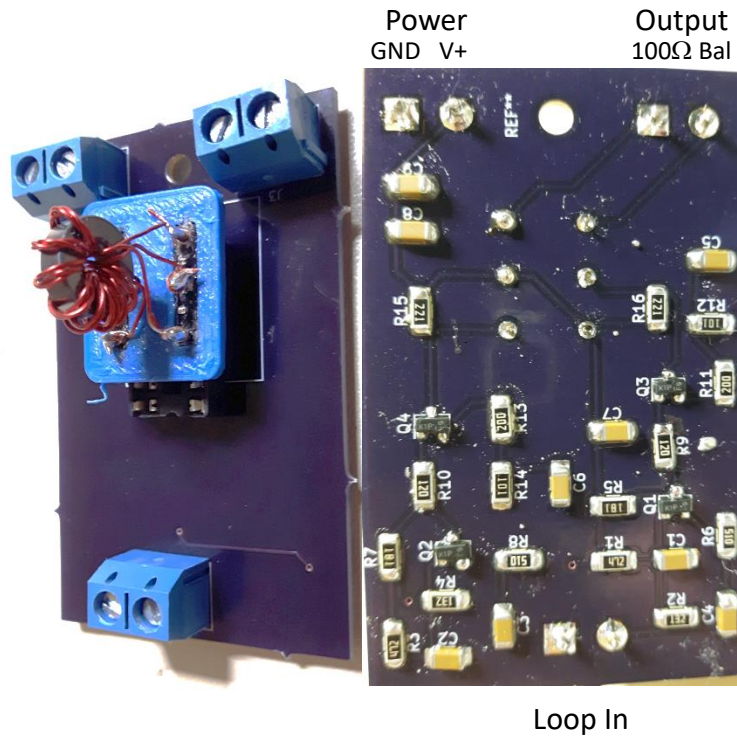

V(sig_in+)/I(C1)

Input Impedance (LTSpice)

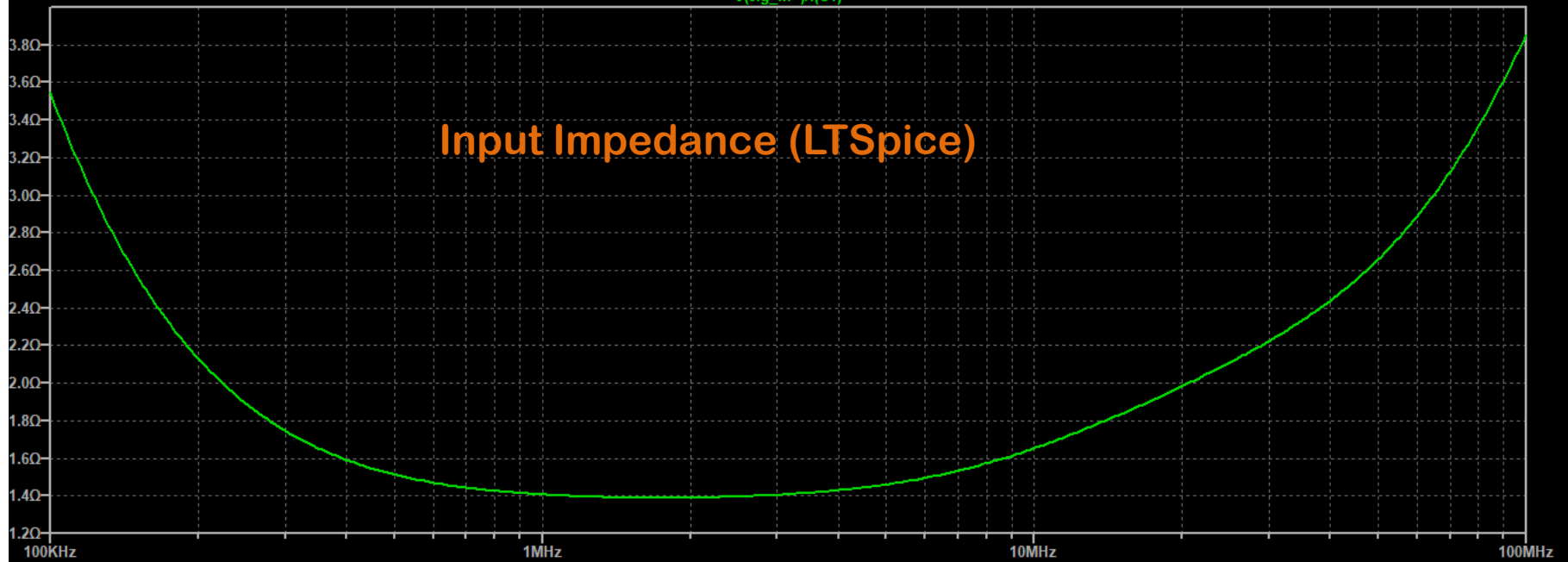

V(out+)

Amplifier Output (LTSpice)

